

EECS 141 – S02

Lecture 7

Inverter Sizing



Digital Integrated Circuits

Inverter

© Prentice Hall 1999

Last Lecture

- The CMOS Inverter: Dynamic Behavior
 - » Capacitors in MOS transistors
- Summary:
 - » Gate Capacitances (Thin Oxide)
 - Channel - voltage-dependent
 - Overlap - constant
 - » Drain- and Source Junction (Depletion)
 - Bottom - CJ, MJ
 - Side-wall - CJSW, MJSW

Digital Integrated Circuits


Inverter

© Prentice Hall 1999


Today

- Propagation Delay
- CMOS Inverter sizing for optimum delay

Propagation Delay

 

 CMOS Inverter Propagation Delay Approach 1




Digital Integrated Circuits

Inverter

© Prentice Hall 1999

 CMOS Inverter Propagation Delay Approach 2




Digital Integrated Circuits

Inverter

© Prentice Hall 1999


CMOS Inverters

 

Digital Integrated Circuits

© Prentice Hall 1999

Transient Response

 

Digital Integrated Circuits


Inverter

© Prentice Hall 1999


Design for Performance

- Keep capacitances small
- Increase transistor sizes
 - » watch out for self-loading!
- Increase V_{DD} (????)


Delay as a function of V_{DD}

 


Device Sizing

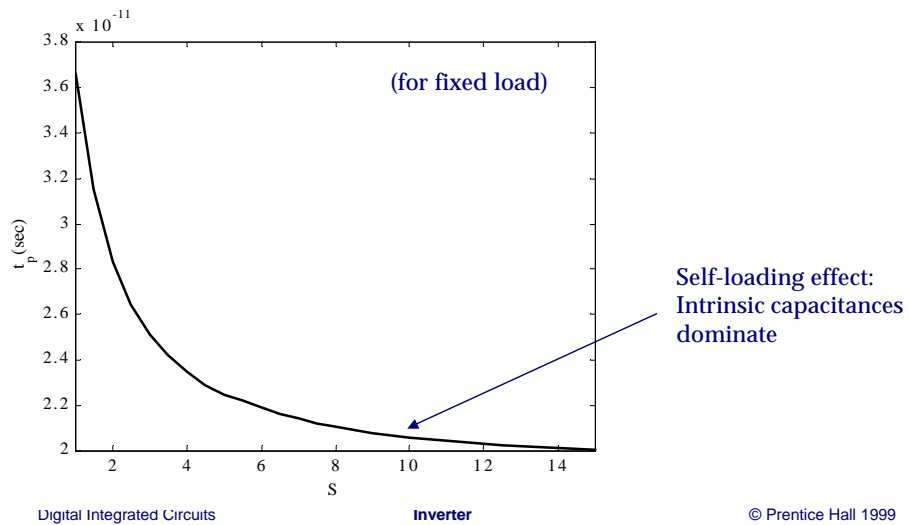

NMOS/PMOS ratio

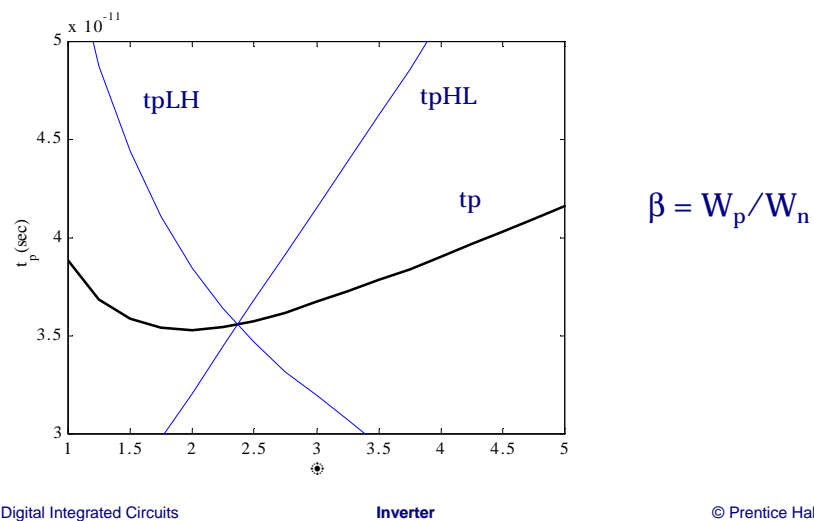

Impact of Rise Time on Delay

 

$$t_{pHL} = \sqrt{t_{pHL(step)}^2 + (t_r/2)^2}$$

Digital Integrated Circuits

Inverter

© Prentice Hall 1999

Inverter Sizing




Digital Integrated Circuits

Inverter

© Prentice Hall 1999

Inverter Chain

 


If C_L is given:

- How many stages are needed to minimize the delay?
- How to size the inverters?

May need some additional constraints.

Inverter Delay

 - Minimum length devices, $L=0.25\mu\text{m}$
- Assume that for $W_P = 2W_N = 2W$
 - same pull-up and pull-down currents
 - approx. equal resistances $R_N = R_P$
 - approx. equal rise t_{pLH} and fall t_{pHL} delays
- Analyze as an RC network




$$R_P = R_{unit} \left(\frac{W_P}{W_{unit}} \right)^{-1} \approx R_{unit} \left(\frac{W_N}{W_{unit}} \right)^{-1} = R_N = R_W$$

$$\text{Delay (D): } t_{pHL} = (\ln 2) R_N C_L \quad t_{pLH} = (\ln 2) R_P C_L$$

$$\text{Load for the next stage: } C_{gin} = 3 \frac{W}{W_{unit}} C_{unit}$$

Inverter with Load

 

k is a constant, equal to 0.69

Assumptions: no load \rightarrow zero delay


$$W_{unit} = 1$$

Digital Integrated Circuits

Inverter

© Prentice Hall 1999

Inverter with Load

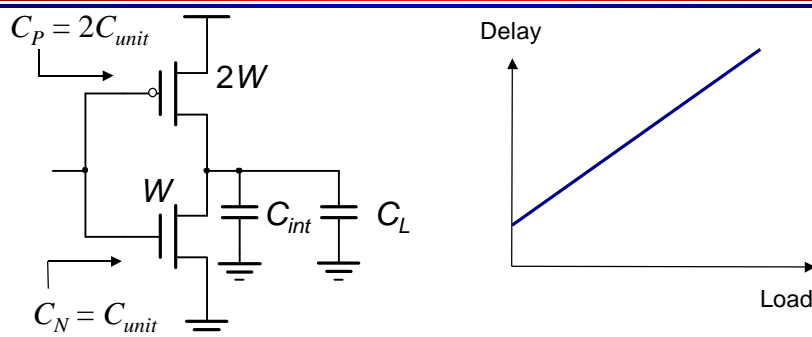

$$\begin{aligned} \text{Delay} &= kR_W(C_{int} + C_L) = kR_W C_{int} + kR_W C_L = kR_W C_{int}(1 + C_L / C_{int}) \\ &= \text{Delay (Internal)} + \text{Delay (Load)} \end{aligned}$$

Digital Integrated Circuits

Inverter

© Prentice Hall 1999

Delay Formula

$$\text{Delay} \sim R_W (C_{int} + C_L)$$

$$t_p = kR_W C_{int} (1 + C_L / C_{int}) = t_{p0} (1 + f / g)$$

$$C_{int} = gC_{gin} \text{ with } g \gg 1$$

$$f = C_L / C_{gin} - \text{effective fanout}$$

$$R = R_{unit} / W ; C_{int} = WC_{unit}$$


$$t_{p0} = 0.69 R_{unit} C_{unit}$$

Digital Integrated Circuits

Inverter

© Prentice Hall 1999

Apply to Inverter Chain

 

$$t_p = t_{p1} + t_{p2} + \dots + t_{pN}$$

$$t_{pj} \sim R_{unit} C_{unit} \left(1 + \frac{C_{gin,j+1}}{gC_{gin,j}} \right)$$

$$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{i=1}^N \left(1 + \frac{C_{gin,j+1}}{gC_{gin,j}} \right) C_{gin,N+1} = C_L$$

Digital Integrated Circuits

Inverter

© Prentice Hall 1999

Optimal Tapering for Given N

Delay equation has $N - 1$ unknowns, $C_{gin,2} - C_{gin,N}$

Minimize the delay, find $N - 1$ partial derivatives

Result: $C_{gin,j+1}/C_{gin,j} = C_{gin,j}/C_{gin,j-1}$

Size of each stage is the geometric mean of two neighbors

$$C_{gin,j} = \sqrt{C_{gin,j-1} C_{gin,j+1}}$$

- each stage has the same effective fanout (C_{out}/C_{in})
- each stage has the same delay

Optimum Delay and Number of Stages

When each stage is sized by f and has same eff. fanout f :

$$f^N = F = C_L / C_{gin,1}$$


Effective fanout of each stage:

$$f = \sqrt[N]{F}$$

Minimum path delay

$$t_p = N t_{p0} \left(1 + \sqrt[N]{F} / g \right)$$

Example

 

C_L/C_1 has to be evenly distributed across $N = 3$ stages:

$$f = \sqrt[3]{8} = 2$$

Optimum Number of Stages

For a given load, C_L and given input capacitance C_{in}
Find optimal sizing f

$$C_L = F \cdot C_{in} = f^N C_{in} \text{ with } N = \frac{\ln F}{\ln f}$$

$$t_p = N t_{p0} \left(F^{1/N} / g + 1 \right) = \frac{t_{p0} \ln F}{g} \left(\frac{f}{\ln f} + \frac{g}{\ln f} \right)$$

$$\frac{\partial t_p}{\partial f} = \frac{t_{p0} \ln F}{g} \cdot \frac{\ln f - 1 - g/f}{\ln^2 f} = 0$$


For $g = 0$, $f = e$, $N = \ln F$

$$f = \exp(1 + g/f)$$

Optimum Effective Fanout f

Optimum f for given process defined by γ

$$f = \exp(1 + g/f)$$

 

$f_{opt} = 3.6$
for $\gamma=1$


Digital Integrated Circuits

Inverter


© Prentice Hall 1999

Impact of Self-Loading on tp

No Self-Loading, $\gamma=0$

 

With Self-Loading $\gamma=1$

 

Digital Integrated Circuits

Inverter

© Prentice Hall 1999

Normalized delay function of F

$$t_p = Nt_{p0} \left(1 + \sqrt[N]{F/g} \right)$$





F	Unbuffered	Two Stage	Inverter Chain
10	11	8.3	8.3
100	101	22	16.5
1000	1001	65	24.8
10,000	10,001	202	33.1

Digital Integrated Circuits

Inverter

© Prentice Hall 1999

Buffer Design

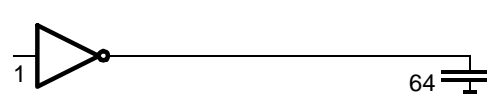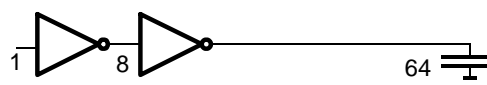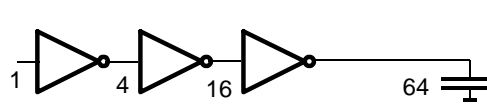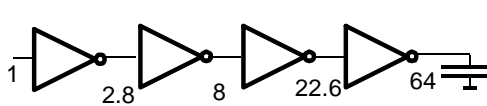	N	f	t_p
	1	64	65
	2	8	18
	3	4	15
	4	2.8	15.3

Digital Integrated Circuits

Inverter

© Prentice Hall 1999